

1

We name the currents I_1 , I_2 , and I_3 as shown.

$$[1] \quad 70.0 - 60.0 - I_2(3.00 \text{ k}\Omega) - I_1(2.00 \text{ k}\Omega) = 0$$

$$[2] \quad 80.0 - I_3(4.00 \text{ k}\Omega) - 60.0 - I_2(3.00 \text{ k}\Omega) = 0$$

$$[3] \quad I_2 = I_1 + I_3$$

- (a) Substituting for I_2 and solving the resulting simultaneous equations yields

$$I_1 = \boxed{0.385 \text{ mA}} \quad (\text{through } R_1)$$

$$I_3 = \boxed{2.69 \text{ mA}} \quad (\text{through } R_3)$$

$$I_2 = \boxed{3.08 \text{ mA}} \quad (\text{through } R_2)$$

- (b) $\Delta V_{ef} = -60.0 \text{ V} - (3.08 \text{ mA})(3.00 \text{ k}\Omega) = \boxed{-69.2 \text{ V}}$

Point e is at higher potential.

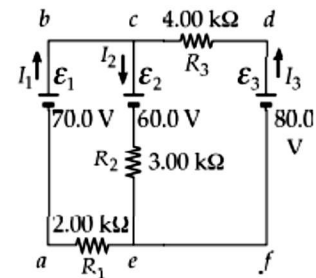


FIG. P28.24

2

65. In the steady state situation, the capacitor voltage will equal the voltage across $R_2 = 15 \text{ k}\Omega$:

$$V_0 = R_2 \frac{\mathcal{E}}{R_1 + R_2} = (15.0 \text{ k}\Omega) \left(\frac{20.0 \text{ V}}{10.0 \text{ k}\Omega + 15.0 \text{ k}\Omega} \right) = 12.0 \text{ V}.$$

Now, multiplying Eq. 27-39 by the capacitance leads to $V = V_0 e^{-t/RC}$ describing the voltage across the capacitor (and across $R_2 = 15.0 \text{ k}\Omega$) after the switch is opened (at $t = 0$). Thus, with $t = 0.00400 \text{ s}$, we obtain

$$V = (12) e^{-0.004 / (15000)(0.4 \times 10^{-6})} = 6.16 \text{ V}.$$

Therefore, using Ohm's law, the current through R_2 is $6.16 / 15000 = 4.11 \times 10^{-4} \text{ A}$.

3.

P29.66 Let v_x and v_\perp be the components of the velocity of the positron parallel to and perpendicular to the direction of the magnetic field.

- (a) The pitch of trajectory is the distance moved along x by the positron during each period, T (see Equation 29.15)

$$p = v_x T = (v \cos 85.0^\circ) \left(\frac{2\pi m}{Bq} \right)$$

$$p = \frac{(5.00 \times 10^6)(\cos 85.0^\circ)(2\pi)(9.11 \times 10^{-31})}{0.150(1.60 \times 10^{-19})} = \boxed{1.04 \times 10^{-4} \text{ m}}$$

- (b) From Equation 29.13, $r = \frac{mv_\perp}{Bq} = \frac{mv \sin 85.0^\circ}{Bq}$

$$r = \frac{(9.11 \times 10^{-31})(5.00 \times 10^6)(\sin 85.0^\circ)}{(0.150)(1.60 \times 10^{-19})} = \boxed{1.89 \times 10^{-4} \text{ m}}$$

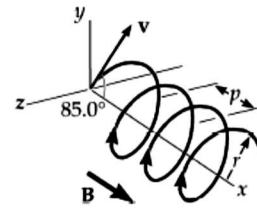


FIG. P29.66

4.

Consider a longitudinal filament of the strip of width dr as shown in the sketch. The contribution to the field at point P due to the current dI in the element dr is

$$dB = \frac{\mu_0 dI}{2\pi r}$$

where $dI = I \left(\frac{dr}{w} \right)$

$$B = \int dB = \int_b^{b+w} \frac{\mu_0 I dr}{2\pi w r} \hat{\mathbf{k}} = \boxed{\frac{\mu_0 I}{2\pi w} \ln \left(1 + \frac{w}{b} \right) \hat{\mathbf{k}}}$$

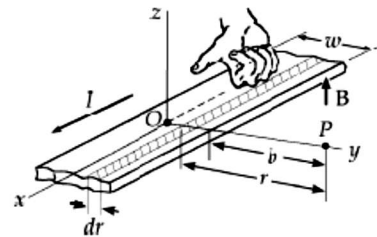


FIG. P30.49

5.

For a counterclockwise trip around the left-hand loop, with $B = At$

$$\frac{d}{dt} [At(2a^2) \cos 0^\circ] - I_1(5R) - I_{PQ}R = 0$$

and for the right-hand loop,

$$\frac{d}{dt} [Aa^2] + I_{PQ}R - I_2(3R) = 0$$

where $I_{PQ} = I_1 - I_2$ is the upward current in QP .

$$\text{Thus, } 2Aa^2 - 5R(I_{PQ} + I_2) - I_{PQ}R = 0$$

$$\text{and } Aa^2 + I_{PQ}R = I_2(3R)$$

$$2Aa^2 - 6RI_{PQ} - \frac{5}{3}(Aa^2 + I_{PQ}R) = 0$$

$$I_{PQ} = \frac{Aa^2}{23R} \text{ upward, and since } R = (0.100 \text{ } \Omega/\text{m})(0.650 \text{ m}) = 0.0650 \text{ } \Omega$$

$$I_{PQ} = \frac{(1.00 \times 10^{-3} \text{ T/s})(0.650 \text{ m})^2}{23(0.0650 \text{ } \Omega)} = \boxed{283 \text{ } \mu\text{A upward}}$$

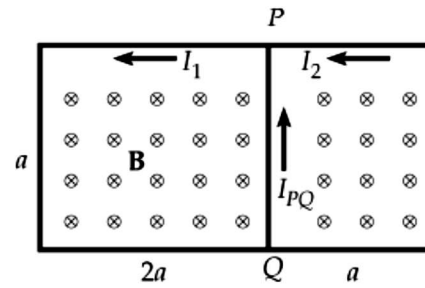


FIG. P31.11